
EE 334 - Homework 4 Report

Aras Güngöre - 2018401117

Ertuğrul Tatlı - 2018401081

1)

$$R_{sig} = 1 \text{ k}\Omega, \quad R_1 = 33 \text{ k}\Omega, \quad R_2 = 17 \text{ k}\Omega, \quad R_C = 2 \text{ k}\Omega, \quad R_E = 1 \text{ k}\Omega, \quad R_L = 10 \text{ k}\Omega$$

$$C_{C1} = 10 \text{ }\mu\text{F}, \quad C_{C2} = 10 \text{ }\mu\text{F}, \quad C_E = 10 \text{ }\mu\text{F}$$

$$I_C = 1.00792 \text{ mA}, \quad I_B = 4.08791 \text{ }\mu\text{A}, \quad I_E = 1.01201 \text{ mA}, \quad V_T = 26 \text{ mV}$$

$$R_B = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{33k \cdot 17k}{33k + 17k} = \boxed{11.22 \text{ k}\Omega = R_B}$$

$$\beta_{DC} = \frac{I_C}{I_B} = \frac{1.00792 \text{ mA}}{4.08791 \text{ }\mu\text{A}} = \boxed{246.561 = \beta_{DC}}, \quad g_{mDC} = \frac{I_C}{V_T} = \frac{1.00792 \text{ mA}}{26 \text{ mV}} = \boxed{38.7662 \text{ mS} = g_{mDC}}$$

$$\beta = \beta_{AC} = \boxed{294 = \beta}, \quad g_m = g_{mAC} = \boxed{24.5 \text{ mS} = g_m}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{294}{24.5 \text{ mS}} = \boxed{12 \text{ k}\Omega = r_\pi}$$

$$R_{in1} = R_B || r_\pi = \frac{R_B r_\pi}{R_B + r_\pi} = \frac{11.22k \cdot 12k}{11.22k + 12k} = \boxed{5.79845 \text{ k}\Omega = R_{in1}}$$

$$R_{in2} = R_B || (r_\pi + (\beta + 1)R_E) = \frac{R_B (r_\pi + (\beta + 1)R_E)}{R_B + (r_\pi + (\beta + 1)R_E)} = \frac{11.22k \cdot (12k + 295 \cdot 1k)}{11.22k + (12k + 295 \cdot 1k)} \\ = \boxed{10.8244 \text{ k}\Omega = R_{in2}}$$

$$\omega_{P1_1} = \frac{1}{C_{C1}(R_{in1} + R_{sig})} = \frac{1}{10\mu \cdot (5.79845k + 1k)} = \boxed{14.7092 \frac{\text{rad}}{\text{s}} = \omega_{P1_1}}$$

$$\omega_{P1_2} = \frac{1}{C_{C1}(R_{in2} + R_{sig})} = \frac{1}{10\mu \cdot (10.8244k + 1k)} = \boxed{8.45709 \frac{\text{rad}}{\text{s}} = \omega_{P1_2}}$$


$$\omega_{P2} = \frac{1}{C_{C2}(R_C + R_L)} = \frac{1}{10\mu \cdot (2k + 10k)} = \boxed{8.33333 \frac{\text{rad}}{\text{s}} = \omega_{P2}}$$

$$\omega_Z = \frac{1}{R_E C_E} = \frac{1}{1k \cdot 10\mu} = \boxed{100 \frac{\text{rad}}{\text{s}} = \omega_Z}$$

$$\omega_{P3_1} = \frac{1}{C_E \left[R_E \parallel \frac{r_\pi + (R_B \parallel R_{sig})}{\beta + 1} \right]} = \frac{1}{10\mu \cdot \left[1k \parallel \frac{12k + (11.22k \parallel 1k)}{295} \right]} = \boxed{2383.61 \frac{rad}{s} = \omega_{P3_1}}$$

$$\omega_{P3_2} = \frac{1}{C_E \left[R_E \parallel \frac{r_\pi + R_B}{\beta + 1} \right]} = \frac{1}{10\mu \cdot \left[1k \parallel \frac{12k + 11.22k}{295} \right]} = \boxed{1370.46 \frac{rad}{s} = \omega_{P3_2}}$$

2)

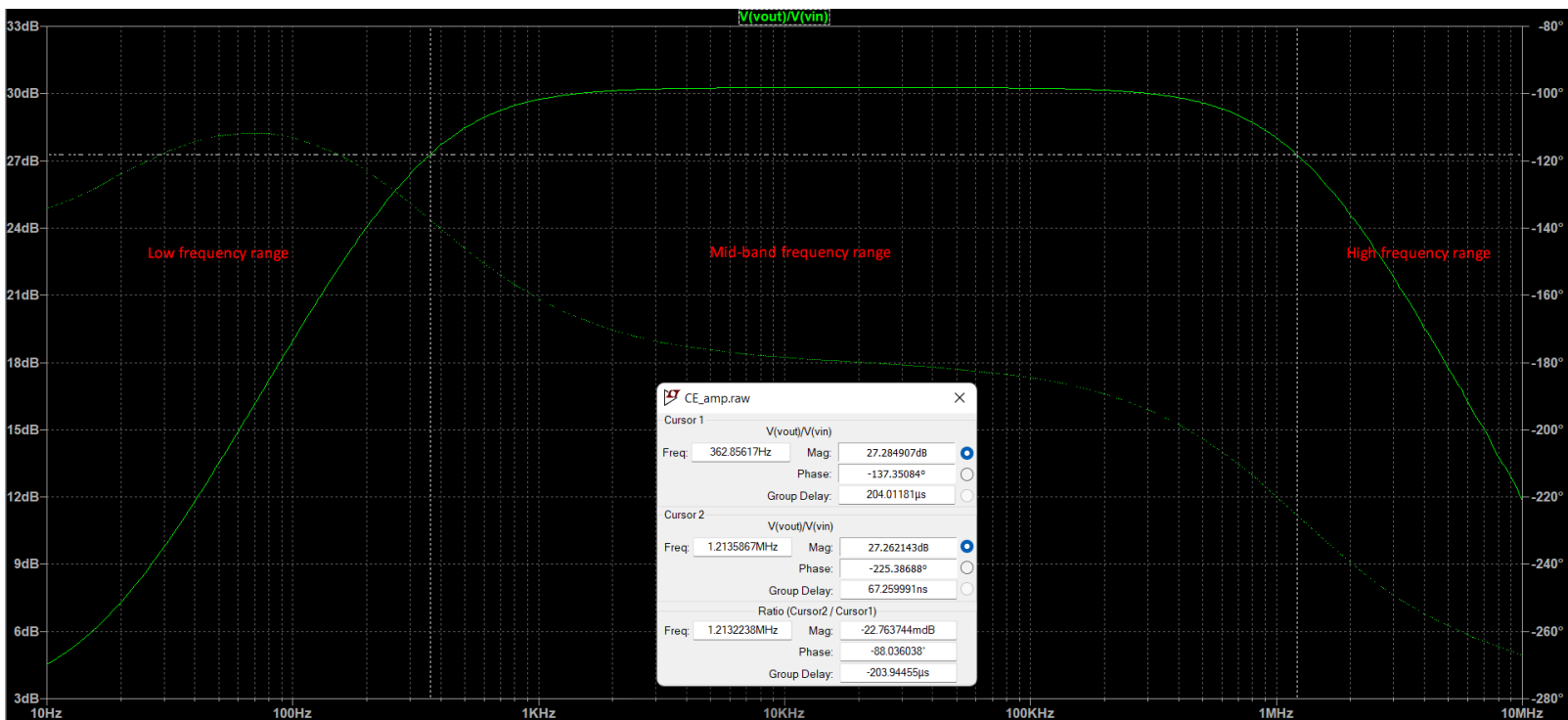


Low frequency range is between 10 Hz and around 363 Hz.


Mid-band frequency range is between around 363 Hz and around 1.21 MHz.

High frequency range is between around 1.21 MHz and 10 MHz.


3)

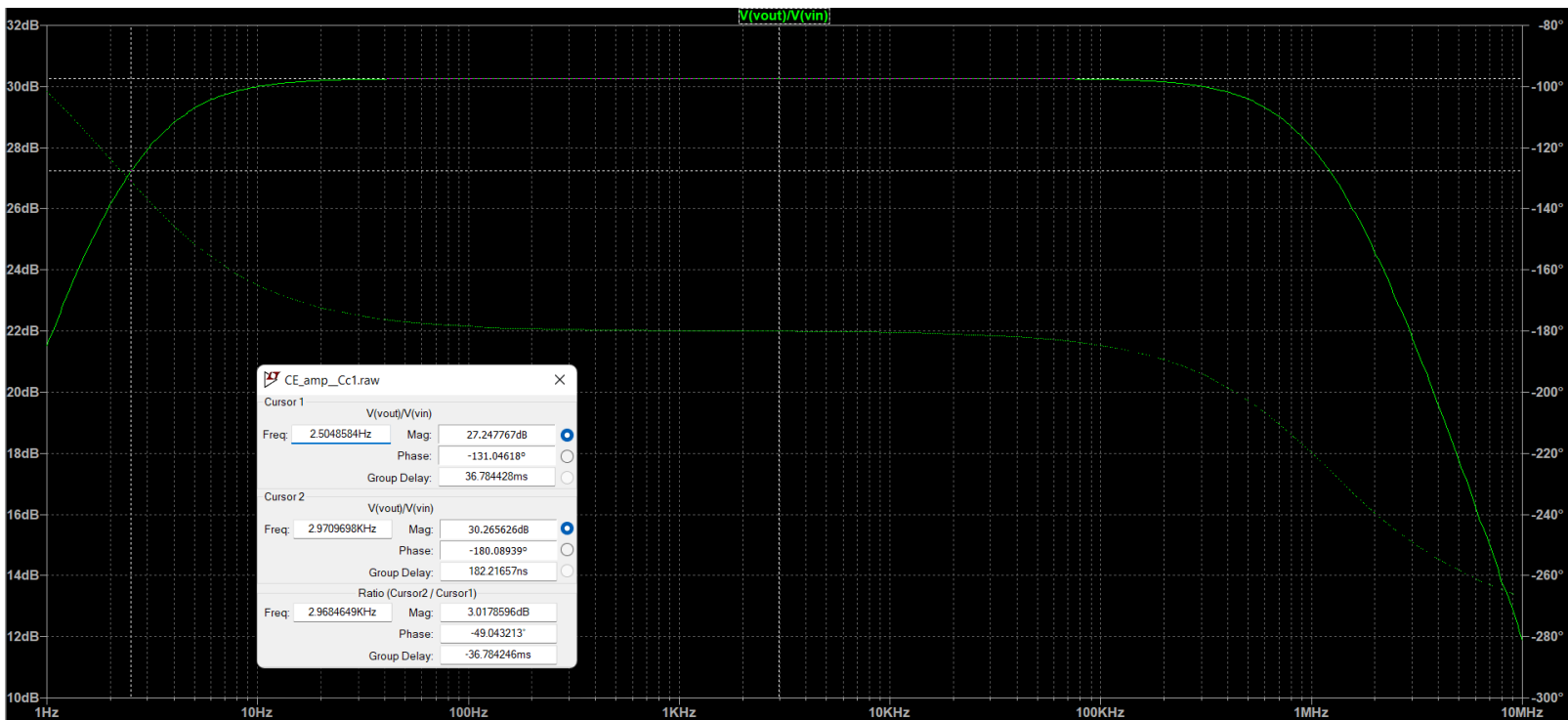

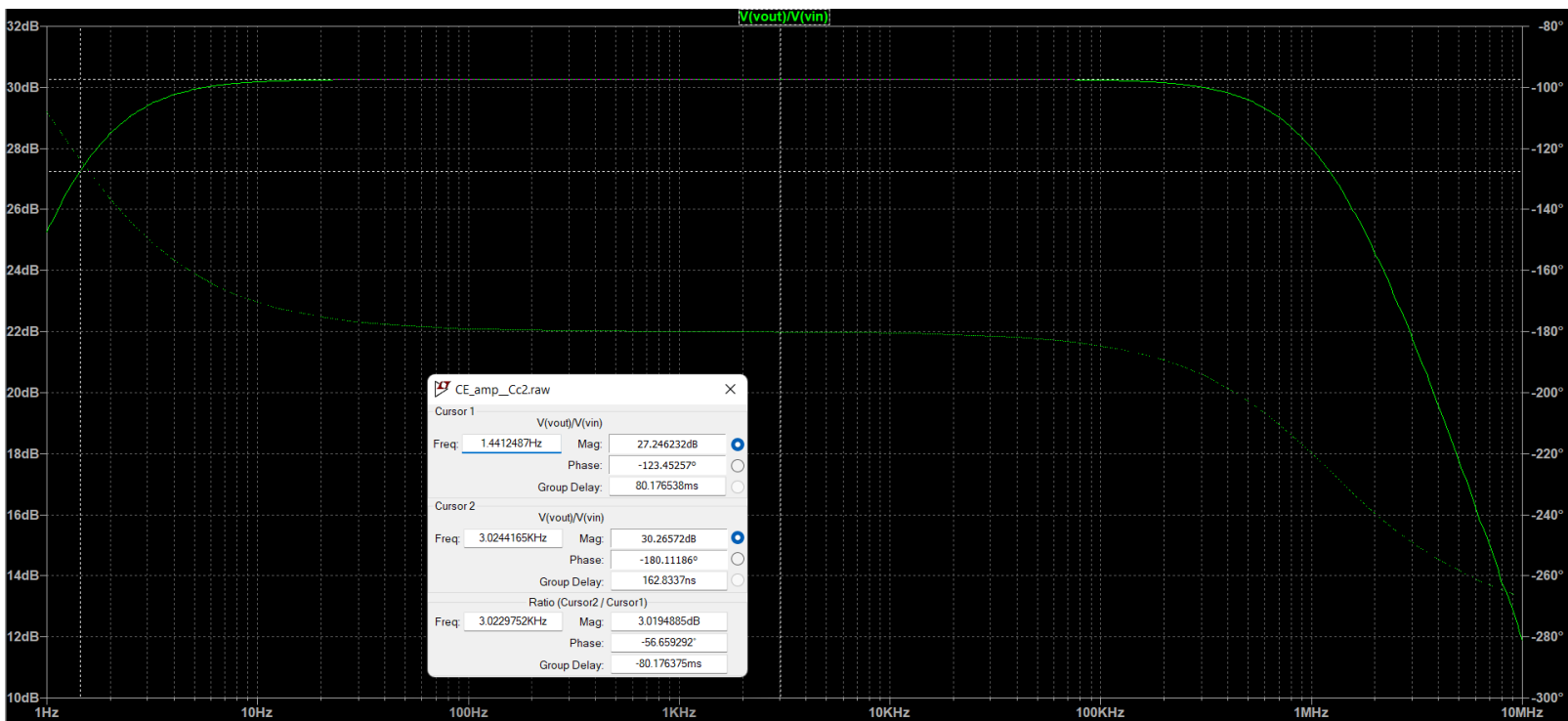For $C_{C1} = 10 \mu\text{F}$ and $C_{C2} = C_E = 10 \text{ mF}$, $f_L \cong 2.51 \text{ Hz}$.



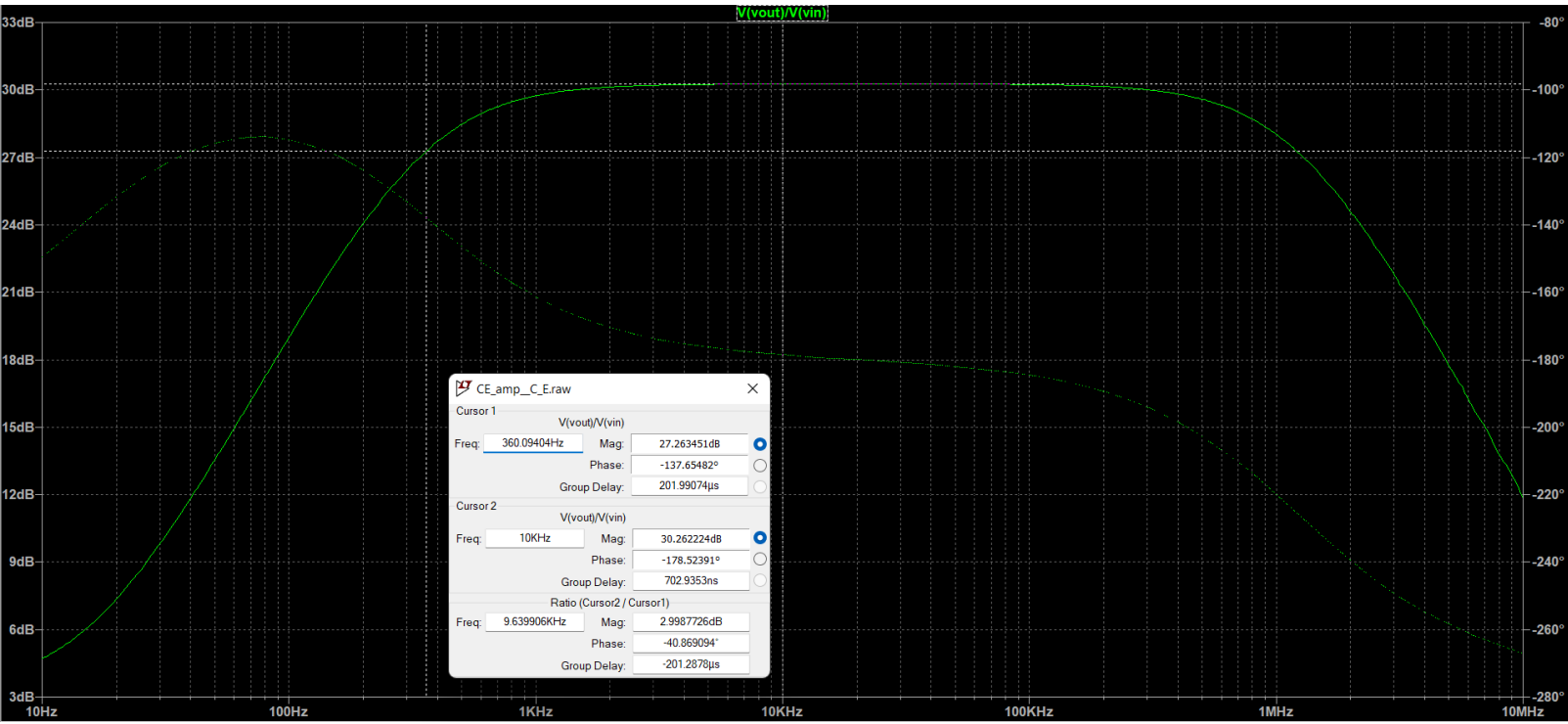For $C_{C2} = 10 \mu\text{F}$ and $C_{C1} = C_E = 10 \text{ mF}$, $f_L \cong 1.44 \text{ Hz}$.



For $C_E = 10 \mu\text{F}$ and $C_{C1} = C_{C2} = 10 \text{ mF}$, $f_L \cong 360 \text{ Hz}$.

4)

$$f_L = 50 \text{ Hz}, \quad \tau_{C1} = C_{C1}R_{C1}, \quad \tau_{CE} = C_ER_{CE}, \quad \tau_{C2} = C_{C2}R_{C2}$$

$$\omega_L = 2\pi f_L = 2\pi \left(\frac{1}{\tau_{C1}} + \frac{1}{\tau_{CE}} + \frac{1}{\tau_{C2}} \right) = 2\pi \left(\frac{1}{C_{C1}R_{C1}} + \frac{1}{C_ER_{CE}} + \frac{1}{C_{C2}R_{C2}} \right) = 2 \cdot 3.141592 \cdot 50$$

$$= \boxed{314.159 \frac{\text{rad}}{\text{s}} = \omega_L}$$

$$R_{C1} = (R_B || r_\pi) + R_{sig} = (R_B || r_\pi) + R_{sig} = (11.22\text{k} || 12\text{k}) + 1\text{k} = \boxed{6.79845 \text{ k}\Omega = R_{C1}},$$

$$R_{CE} = R_E || \left[\frac{r_\pi + R_B || R_{sig}}{\beta + 1} \right] = 1\text{k} || \left[\frac{12\text{k} + 11.22\text{k} || 1\text{k}}{295} \right] = \boxed{41.9532 \Omega = R_{CE}},$$

$$R_{C2} = R_C + R_L = 10\text{k} + 2\text{k} = \boxed{12 \text{ k}\Omega = R_{C2}}$$

Selecting C_E so that it contributes 80% of the value of ω_L gives:


$$\frac{1}{C_ER_{CE}} = 0.8\omega_L \implies C_E = \frac{1}{0.8R_{CE}\omega_L} = \frac{1}{0.8 \cdot 41.9532 \cdot 100} = \boxed{94.8407 \mu\text{F} = C_E}$$

Selecting C_{C1} so that it contributes 10% of the value of ω_L gives:

$$\frac{1}{C_{C1}R_{C1}} = 0.1\omega_L \implies C_{C1} = \frac{1}{0.1R_{C1}\omega_L} = \frac{1}{0.1 \cdot 6.79845\text{k} \cdot 100} = \boxed{4.6821 \mu\text{F} = C_{C1}}$$

Selecting C_{C2} so that it contributes 10% of the value of ω_L gives:

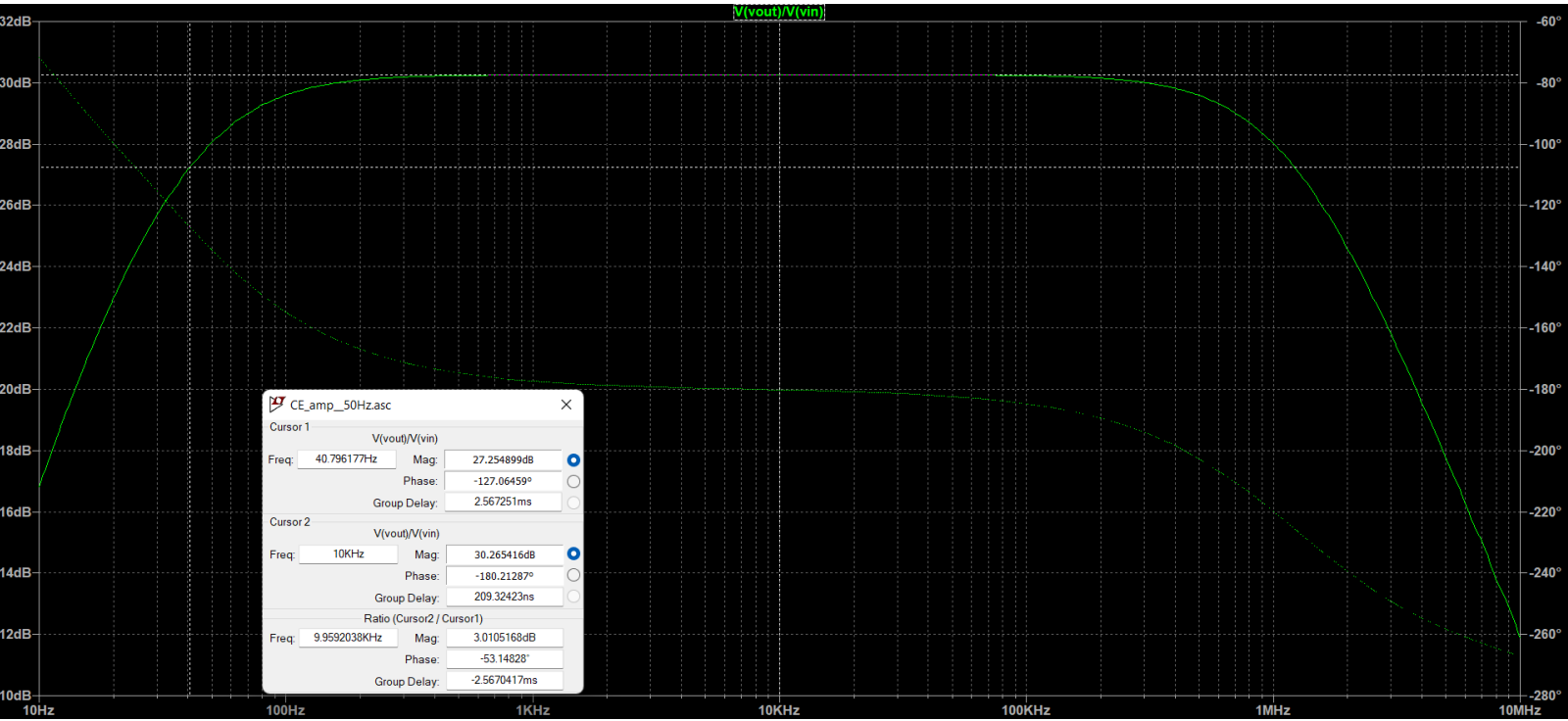
$$\frac{1}{C_{C2}R_{C2}} = 0.1\omega_L \implies C_{C2} = \frac{1}{0.8R_{C2}\omega_L} = \frac{1}{0.1 \cdot 12k \cdot 100} = \boxed{2.65258 \mu F = C_{C2}}$$



For $C_{C1} = 4.6821 \mu F$, $C_{C2} = 2.65258 \mu F$, and $C_E = 94.8407 \mu F$; $f_L \cong 40.8 \text{ Hz}$.

Selecting C_E so that it contributes 10 times of C_{C1} and C_{C2} gives:
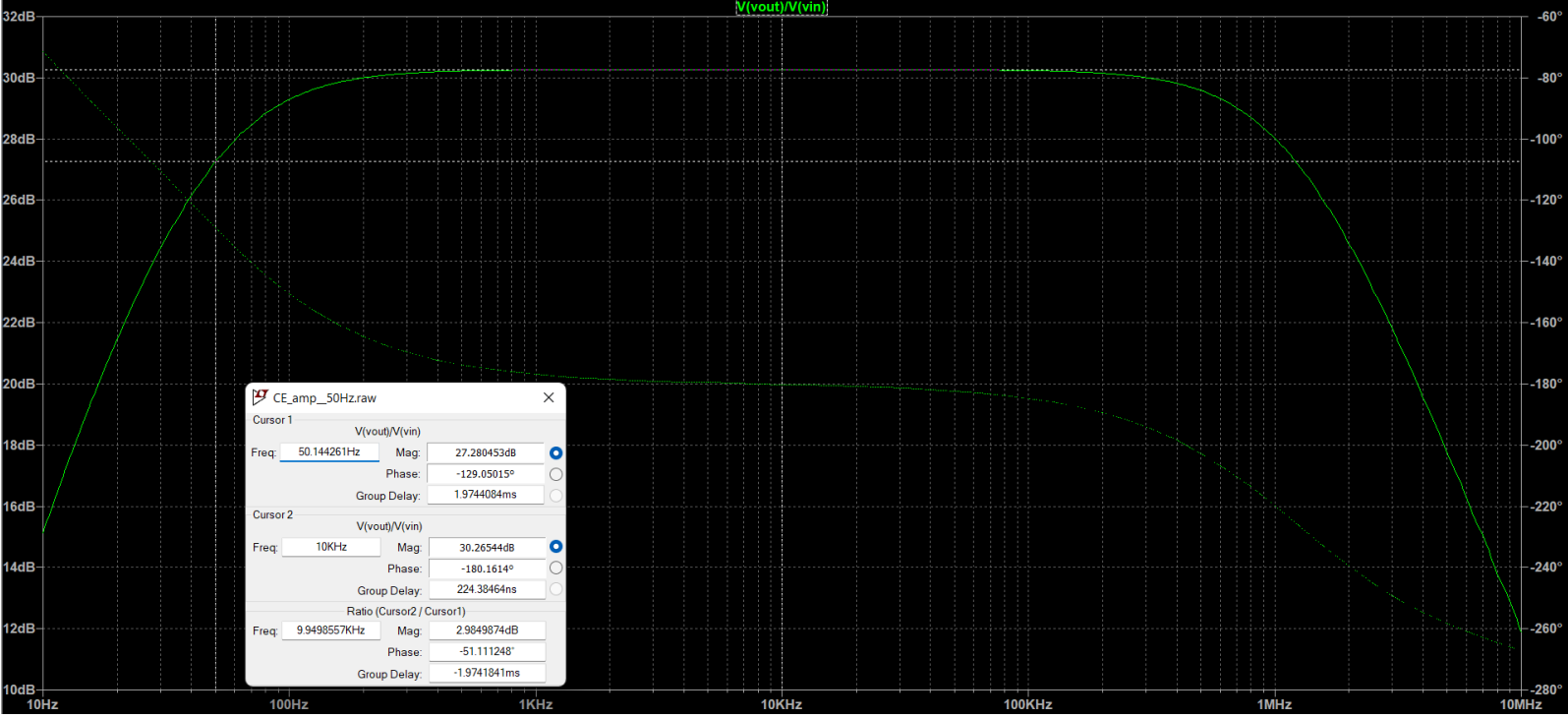
$$\frac{1}{C_E R_{CE}} = \omega_L \implies C_E = \frac{1}{R_{CE} \omega_L} = \frac{1}{41.9532 \cdot 100} = \boxed{75.8725 \mu F = C_E}$$




For $C_{C1} = 4.6821 \mu F$, $C_{C2} = 2.65258 \mu F$, and $C_E = 75.8725 \mu F$; $f_L \cong 50$ Hz.

5)

$$\omega_Z = \omega_{P1_1} = \frac{1}{C_{C1_1}(R_{in1} + R_{sig})} \implies C_{C1_1} = \frac{1}{\omega_Z(R_{in1} + R_{sig})} = \frac{1}{100 \cdot (5.79845k + 1k)} = \boxed{1.47092 \mu F = C_{C1_1}}$$

$$\omega_Z = \omega_{P1_2} = \frac{1}{C_{C1_2}(R_{in2} + R_{sig})} \implies C_{C1_2} = \frac{1}{\omega_Z(R_{in2} + R_{sig})} = \frac{1}{100 \cdot (10.8244k + 1k)} = \boxed{845.709 nF = C_{C1_2}}$$
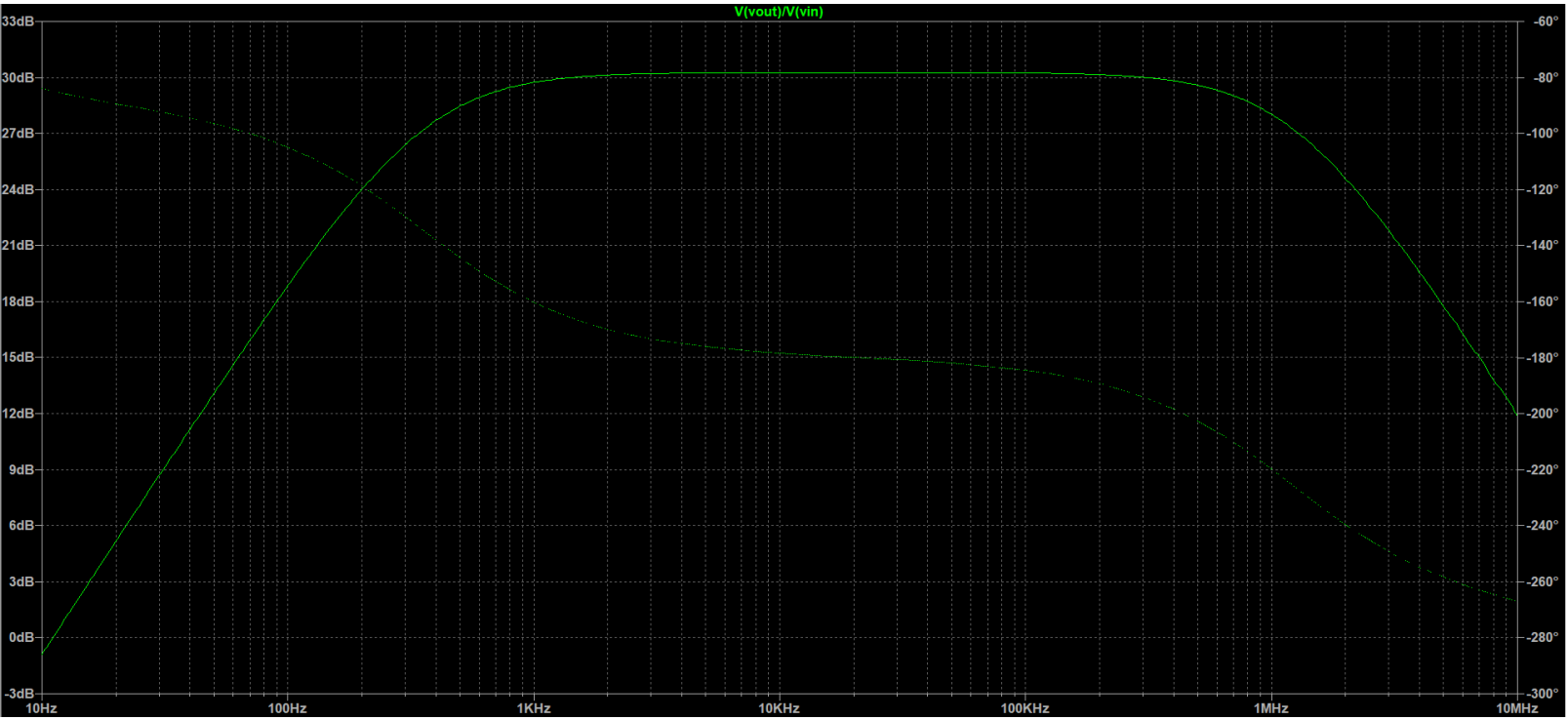
$$\omega_Z = \omega_{P2} = \frac{1}{C_{C2}(R_C + R_L)} \implies C_{C2} = \frac{1}{\omega_Z(R_C + R_L)} = \frac{1}{100 \cdot (2k + 10k)} = \boxed{833.333 nF = C_{C2}}$$



For $C_{C2} = 833.333 \text{ nF}$ and $C_{C1} = C_E = 10 \text{ }\mu\text{F}$, since ω_Z is cancelled with ω_{P2} , we observe that there is a more linear dB gain increase in the low frequency region.